

INTRODUCTION:

SSRs (solid-state relays) have no movable contacts. SSRs are not very different in general operation from mechanical relays that have movable contacts. SSRs, however, employ semiconductor switching elements, such as thyristors, triacs, diodes, and transistors. Furthermore, SSRs employ optical semiconductors called photocouplers to isolate input (control) and output (load) signals. Photocouplers change electric signals into optical signals and transmit the signals through space, thus fully isolating the input and output sections while transferring the signals at high speed. SSRs consist of electronic parts with no mechanical contacts. Therefore, SSRs have a variety of features that mechanical relays do not incorporate. The greatest feature of SSRs is that SSRs do not use switching contacts that will physically wear out. SSRs are ideal for a wide range of applications due to the following performance characteristics,

Feature	Electromechanical Relay	Solid State Relay
<i>Switching Element</i>	Mechanical contacts	Semiconductor devices
<i>Moving Parts</i>	Yes (armature, contacts)	No
<i>Switching Speed</i>	Slow (5-15 ms)	Fast (< 1 ms)
<i>Lifespan</i>	Limited (mechanical wear)	Very long
<i>Noise</i>	Audible click	Silent
<i>Contact Bounce</i>	Yes	No
<i>ON Resistance</i>	Very low (mΩ)	Higher (mΩ to Ω)
<i>OFF Resistance</i>	Infinite	High (MΩ)
<i>Heat Dissipation</i>	Low	Higher (needs heatsink)

OBJECTIVES:

- ❖ **Primary Objective:** The primary objective of this project is to design, simulate, and implement a Solid-State Relay (SSR) interface circuit capable of controlling a high-voltage Alternating Current (AC) load (220V/110V) using a low-voltage (3.3V) digital logic signal from an ESP32 microcontroller. The project aims to demonstrate a safe, reliable, and contactless method of switching AC appliances, serving as a foundational module for Home Automation and IoT (Internet of Things) applications.
- ❖ **Implementation of Galvanic Isolation:** To design an isolation stage using the MOC3023 Optocoupler to strictly separate the low-voltage control logic (ESP32) from the high-voltage AC mains. The objective is to ensure that no electrical faults on the load side can propagate back to damage the microcontroller or endanger the user.
- ❖ **Design of Solid-State Switching Mechanism:** To utilize a BTA41-600B Triac as the primary switching element instead of an electromechanical relay. This aims to eliminate mechanical wear and tear, contact bounce, and electromagnetic interference (sparks) associated with traditional relays, thereby achieving a silent and long-lasting switching solution.

- ❖ *Signal Conditioning and Driver Design*: To develop a transistor-based driver stage using a BC547 (NPN) transistor to amplify the weak GPIO current (approx. 12mA required for the optocoupler) from the microcontroller. This ensures the ESP32 operates within safe current limits while reliably triggering the isolation stage.
- ❖ *Interfacing and Logic Control*: To program the ESP32 microcontroller to generate a precise Pulse Width Modulation (PWM) or periodic digital signal (Blinking Logic) to control the state of the AC load. This demonstrates the capability of the system to translate software commands into physical power control.

CIRCUIT OPERATION:

Stage-1. The Controller: ESP32

- Component: ESP32 (U1)
- Action: The "blinking" is created by a program running on the ESP32. This program toggles GPIO13 between a HIGH state (3.3V) and a LOW state (0V) periodically (e.g., on for 1 second, off for 1 second). This pin is the single "command" signal for the entire circuit.

The DC Driver Stage (Low-Voltage Side)

This section's job is to take the weak, low-power signal from the ESP32 and use it to safely turn on the internal light of the optocoupler.

- Component: BC547 (NPN Transistor)
- Role: This is a low-side switch. The ESP32's GPIO pin can't (and shouldn't) provide the current needed to drive the optocoupler and indicator LED directly. The transistor acts as a current amplifier: the ESP32 provides a tiny control current to the "Base" of the transistor, which then switches a much larger load current.
- Component: R (68kΩ Resistor)
- Role: This is the base resistor. It protects the ESP32's GPIO pin. When GPIO13 goes HIGH (3.3V), this resistor limits the current flowing into the transistor's base to a very small, safe amount (approx. $(3.3V - 0.7V) / 68,000\Omega \approx 38\mu A$). This tiny current is all that's needed to turn the transistor fully ON.
- Component: R (1kΩ Resistor) & LED 0803_R (Red LED)
- Role: This is your visual indicator. The 1kΩ resistor is a current-limiting resistor for the red LED. When the BC547 switch turns ON, it connects this LED's cathode to ground, completing the circuit: $3.3V \rightarrow 1k\Omega \text{ Resistor} \rightarrow \text{Red LED} \rightarrow \text{BC547} \rightarrow \text{Ground}$. The resistor limits the current to about $(3.3V - 1.8V) / 1000\Omega \approx 1.5mA$, making the LED light up.

- Component: R (220Ω Resistor) & MOC3033 (Internal LED, Pins 1-2)
- Role: This is the actual control signal. The 220Ω resistor is the current-limiting resistor for the infrared (IR) LED inside the MOC3033. When the BC547 turns ON, it completes this circuit: 3.3V → 220Ω Resistor → MOC3033 (Pin 1 to 2) → BC547 → Ground. This resistor sets the MOC's LED current to $(3.3V - 1.2V) / 220\Omega \approx 9.5mA$. This is a strong, reliable current to ensure the optocoupler activates.

Operation of this Stage:

- **When GPIO13 is LOW (0V):**
 1. No current flows to the base of the BC547.
 2. The transistor is OFF (in "cutoff").
 3. It acts like an open switch. No current can flow to ground.
 4. Result: The Red LED is OFF, and the MOC3033's internal IR LED is OFF.
- **When GPIO13 is HIGH (3.3V):**
 1. A small current flows from GPIO13, through the 68kΩ resistor, into the transistor's base.
 2. This turns the transistor ON (in "saturation").
 3. It acts like a closed switch, connecting its collector pin directly to ground.
 4. Result: The Red LED and the MOC3033's IR LED both turn ON.

Stage-2. The Isolation Stage (The Optocoupler)

- Component: MOC3033 (Optocoupler)
- Role: This is the most critical safety component. It provides galvanic isolation. The IR light from the internal LED (pins 1-2) shines across a physical gap onto a light-sensitive detector (pins 4-6). There is no electrical connection between the 3.3V DC side and the high-voltage AC side. This protects the ESP32 and you from the dangerous AC voltage.
- CRITICAL DETAIL: Non-Zero-Crossing Driver
 - As a Non-Zero-Crossing (MOC303x) driver, its internal AC detector will fire *immediately* when the IR LED turns on, regardless of where the AC waveform is (e.g., at its peak voltage).
 - This is in contrast to a Zero-Crossing (MOC304x) driver, which waits for the AC voltage to be near zero before firing.

- Implication: For a resistive load like a bulb, this design will cause a larger in-rush of current and more electrical noise (EMI) than a zero-crossing driver. However, it will still work perfectly fine to blink the bulb.

Stage-3. The AC Power Switching Stage (The "SSR")

This is the high-voltage "business end" of the circuit.

- Component: BTA41-600B (Triac)
- Role: This is the heavy-duty AC switch. A Triac is a component that can switch AC current in both directions. The "BTA41" means it can handle 41 Amps, and the "600B" means it can block 600 Volts. This is massive overkill for a lightbulb, which means it will run very cool and be extremely reliable.
- Component: R (150Ω Resistor)
- Role: This is a current-limiting resistor for the MOC3033's output. When the MOC activates, this resistor, along with the 330Ω gate resistor, limits the peak current that flows out of the AC line and into the Triac's gate. This protects the MOC3033's internal detector from being destroyed by the high-voltage AC.
- Component: R (330Ω Resistor - in series with Gate)
- Role: This is the gate-current limiting resistor. It works with the 150Ω resistor to set the "turn-on" pulse for the Triac. It ensures the gate current is strong enough to trigger the Triac but not so strong that it damages the MOC or the Triac's gate.
- Component: R (330Ω Resistor - from Gate to T1)
- Role: This is a pull-down resistor and is extremely important for reliability. It connects the Triac's Gate (G) to its Main Terminal 1 (T1). Its job is to improve noise immunity. Without this resistor, small voltage spikes or electrical noise on the AC line could accidentally "tickle" the gate and cause the Triac to turn on falsely, making the bulb flicker or stay on. This resistor "shunts" that noise away, ensuring the Triac only turns on when it gets a strong, deliberate signal from the MOC3033.

Operation of this Stage:

- To Turn the Bulb ON (MOC is Active):
 1. The MOC's internal IR LED is ON.
 2. The MOC's internal light detector activates, closing the switch between its pins 6 and 4.
 3. This completes a circuit: AC Line → 150Ω Resistor → MOC (Pin 6 to 4) → 330Ω Gate Resistor → Triac Gate (G).
 4. A pulse of current flows into the Triac's gate.
 5. This "fires" or "triggers" the Triac, turning it ON.

6. The Triac now acts as a closed switch between its T2 and T1 terminals.
 7. Result: A large AC current flows from the AC Source (L), through the load (bulb), through the Triac (T2 to T1), and back to Neutral (N). The bulb turns ON.
- To Turn the Bulb OFF (MOC is Inactive):
1. The MOC's internal IR LED is OFF.
 2. The MOC's output (pins 6-4) is an open circuit.
 3. No trigger current can flow to the Triac's gate.
 4. Important: A Triac is a "latching" device. It will stay on until the main current flowing through it (the bulb's current) drops to zero.
 5. Since this is AC, the current naturally drops to zero 100 or 120 times every second (at every zero-crossing of the AC wave).
 6. The next time the AC current crosses zero, the Triac automatically turns OFF.
 7. Result: Because it's not receiving any new "turn-on" pulses from the MOC, it stays OFF. The circuit is broken. The bulb turns OFF.